
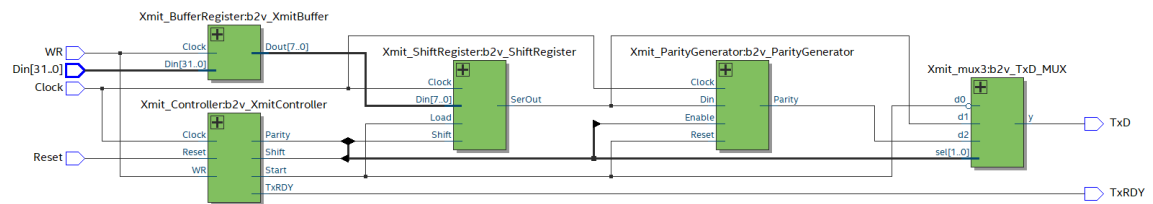



Synthesized Schematic:

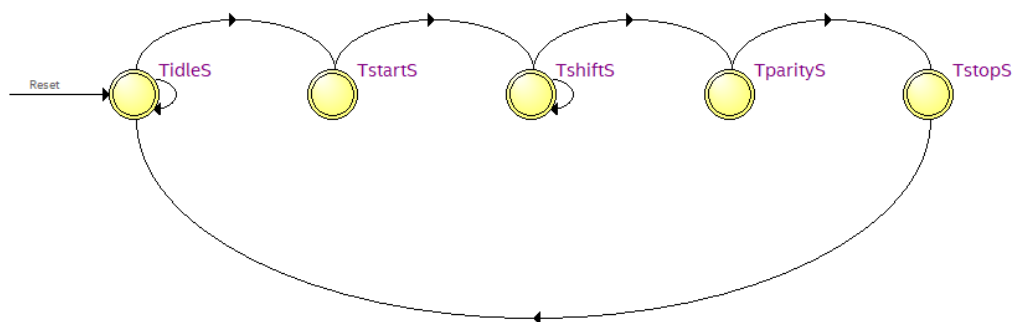

Controller's FSM



Testbench Result for odd number of 1's:

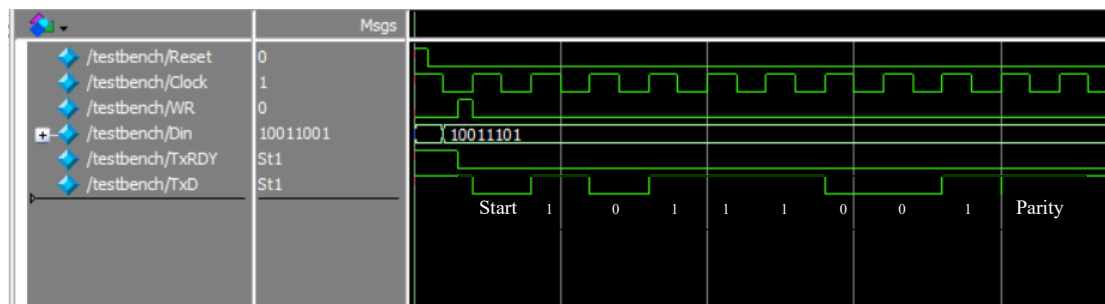

Testbench Result for even number of 1's:

